

Rev 6 Sen 30 2007

Build the phase 90. You must use matched FETs for this circuit to work. Tweaking the value of the zener diode may be needed for some FETs. It's recommended to use sockets for the FETs and zener diode. Also, if using FETs other than those listed, they may need to be rotated 180 degrees, "G" marked pads must match GATE pin on the actual FETs used. Off board wiring except for the potentiometers are not shown on the layout. Trademarks remain property of their owners. Visit www.tonepad.com for more!

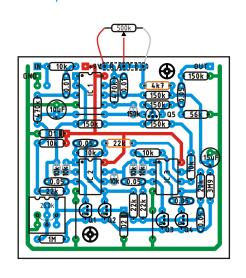

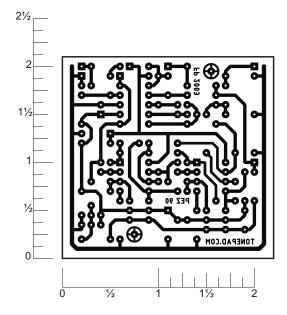


Parts List

1 - 3M9

Resistors	Pots	Diodes
1 - 4k7	1 - 500k rev. Log.	D1 - 1N914
10 - 10k	1 - 250k trim.	D2 - 5.1V zener
5 - 22k	Capacitors	Transistors &ICs
1 - 56k	6 - 0.05 μF	1 - 2N4125
6 - 150k	2 - 0.01 µF	4 - 2N5952 (Matched)
2 - 470k	1 - 10 μĖ	3 - TL072 `
1 - 1M	1 - 15 µF	

Schematic

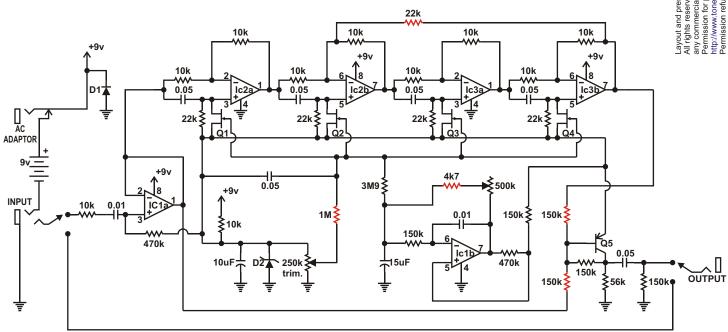

Layout and presentation by Francisco Peña 2001 - 2007®. All rights reserved. Authorization for personal use only, any commercial use is forbidden. Permission for posting/serving limited to http://www.tonepad.com Permission refused for posting from other sites.